

Lab 2: The Design Hierarchy

Qianjun Huang

October 3, 2022

Part I

1. If the truth table in Table 2.1 of the handout was given in full, how many rows would it have? 64
2. Export the schematic of the mux4to1 subcircuit as an image and include it in your report.

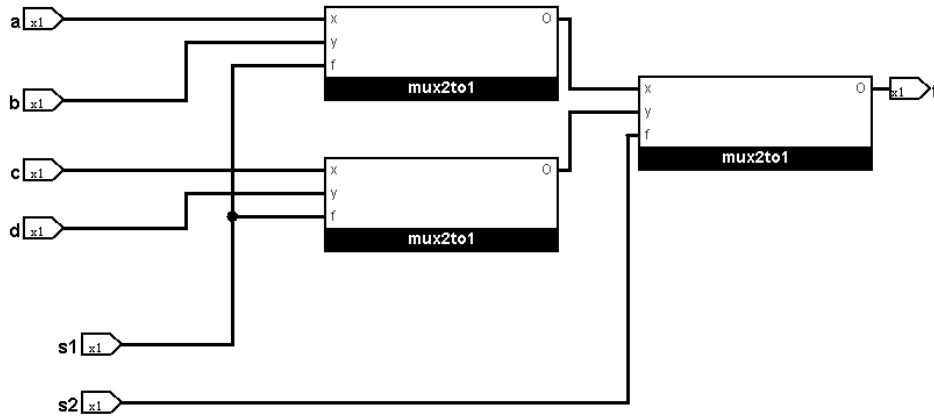


Figure 1: A schematic of the 4-to-1 multiplexer

Part II

1. Derive seven truth tables, one for each segment of the 7-segment decoder.

$D_{3:0}$	Character	S_0	S_1	S_2	S_3	S_4	S_5	S_6
0000	0	1	1	1	1	1	1	0
0001	1	0	1	1	0	0	0	0
0010	2	1	1	0	1	1	0	1
0011	3	1	1	1	1	0	0	1
0100	4	0	1	1	0	0	1	1
0101	5	1	0	1	1	0	1	1
0110	6	1	0	1	1	1	1	1
0111	7	1	1	1	0	0	0	0
1000	8	1	1	1	1	1	1	1
1001	9	1	1	1	1	0	1	1
1010	A	1	1	1	0	1	1	1
1011	b	0	0	1	1	1	1	1
1100	c	0	0	0	1	1	0	1
1101	d	0	1	1	1	1	0	1
1110	E	1	0	0	1	1	1	1
1111	F	1	0	0	0	1	1	1

2. Use Karnaugh maps to write seven Boolean functions for each segment so that they are optimized.

$$\begin{aligned}
S_0 &= \overline{D_2} \cdot \overline{D_0} + \overline{D_3} \cdot D_1 + \overline{D_3} \cdot D_2 \cdot D_0 + D_2 \cdot D_1 + D_3 \cdot \overline{D_2} \cdot \overline{D_1} \\
S_1 &= \overline{D_3} \cdot \overline{D_2} + \overline{D_3} \cdot \overline{D_1} \cdot \overline{D_0} + \overline{D_2} \cdot \overline{D_0} + \overline{D_3} \cdot D_1 \cdot D_0 + D_3 \cdot \overline{D_1} \cdot D_0 \\
S_2 &= \overline{D_3} \cdot \overline{D_1} + \overline{D_3} \cdot D_0 + \overline{D_1} \cdot D_0 + \overline{D_3} \cdot D_2 + D_3 \cdot \overline{D_2} \\
S_3 &= \overline{D_3} \cdot \overline{D_2} \cdot \overline{D_0} + \overline{D_3} \cdot D_1 \cdot \overline{D_0} + \overline{D_2} \cdot D_1 \cdot D_0 + D_2 \cdot \overline{D_1} \cdot D_0 + D_3 \cdot \overline{D_1} + D_3 \cdot D_2 \cdot \overline{D_0} \\
S_4 &= \overline{D_2} \cdot \overline{D_0} + D_1 \cdot \overline{D_0} + D_3 \cdot D_1 + D_3 \cdot D_2 \\
S_5 &= \overline{D_3} \cdot \overline{D_1} \cdot \overline{D_0} + \overline{D_3} \cdot D_2 \cdot \overline{D_1} + \overline{D_3} \cdot D_2 \cdot \overline{D_0} + D_3 \cdot \overline{D_2} + D_3 \cdot D_1 \\
S_6 &= \overline{D_2} \cdot D_1 + D_2 \cdot \overline{D_1} + D_2 \cdot \overline{D_0} + D_3
\end{aligned}$$

3. Use the naming scheme HEX0, HEX1, ..., HEX6 for each subcircuit. Export each subcircuit schematic as an image and include it in your report.

 


Figure 2: A schematic of HEX0

 


Figure 3: A schematic of HEX1

 


Figure 4: A schematic of HEX2

 


Figure 5: A schematic of HEX3

 


Figure 6: A schematic of HEX4

 


Figure 7: A schematic of HEX5

 


Figure 8: A schematic of HEX6